

# Relatório

Tópico: Aula 4 & 5 - Contadores

Grupo: Maicon Chaves Marques 14593530

Pedro Calciolari Jardim 11233668

João Vitor Pereira Candido 13751131

## Parte 1: 8-bits counter

O contador de 8 bits foi implementado utilizando Flip-Flops do tipo T, organizados para alternar seus estados de forma sequencial com base no sinal de *clock*. O funcionamento do contador é estruturado conforme descrito abaixo:

- O sinal **enable1** habilita o funcionamento do contador. Ele permite que os Flip-Flops alternem seus estados conforme o *clock*.
- O sinal **clock** é responsável por coordenar a alternância dos Flip-Flops, sendo aplicado simultaneamente a todos.
- O sinal **clear** é assíncrono e força todos os Flip-Flops a assumirem o estado lógico 0, independente de seu estado atual.
- A contagem é realizada com base em uma lógica de *toggle*: cada Flip-Flop T alterna seu estado dependendo do valor do Flip-Flop imediatamente anterior e do sinal de habilitação (*enable*).

Código VHDL:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity contador_8bits is
```

```
    Port ( enable1 : in STD_LOGIC;      -- Sinal de clock
```

```
          clock : in STD_LOGIC;        -- Sinal de clock
```

```
          clear : in STD_LOGIC;        -- Sinal de clear assíncrono
```

```
          Q0 : out STD_LOGIC;
```

```
          Q1 : out STD_LOGIC;
```

```
          Q2 : out STD_LOGIC;
```

```
          Q3 : out STD_LOGIC;
```

```
          Q4 : out STD_LOGIC;
```

```
          Q5 : out STD_LOGIC;
```

```
          Q6 : out STD_LOGIC;
```

```
          Q7 : out STD_LOGIC
```

```
);
```

```

end contador_8bits;

architecture Behavioral of contador_8bits is
    -- Sinais intermediários para conectar os flip-flops
    signal enable_signals : STD_LOGIC_VECTOR (7 downto 0); -- Estados internos dos
flip-flops
    signal Q_internal : STD_LOGIC_VECTOR (7 downto 0); -- Estados internos dos flip-flops
    signal and_signals : STD_LOGIC_VECTOR (7 downto 0); -- Estados internos dos
flip-flops

    component t_flip_flop is
        port (
            clock : in STD_LOGIC;
            clear : in STD_LOGIC;
            enable : in STD_LOGIC;
            Q : out STD_LOGIC;
            nQ : out STD_LOGIC
        );
    end component;

begin
    -- Instanciando o primeiro flip-flop T (bit menos significativo)
    tff0: t_flip_flop
        port map (clock => clock,
            clear => clear,
            enable => enable1,      -- Flip-flop T sempre habilitado
            Q => Q_internal(0) -- Saída do primeiro flip-flop
        );

    -- Geração dos sinais AND entre os flip-flops
    and_signals(1) <= Q_internal(0) AND enable1; -- O primeiro flip-flop não precisa de AND

    tff1: t_flip_flop
        port map (clock => clock,
            clear => clear,
            enable => and_signals(1), -- O segundo flip-flop alterna quando o primeiro
estiver em '1'
            Q => Q_internal(1)
        );

    -- AND para o próximo flip-flop
    and_signals(2) <= and_signals(1) AND Q_internal(1);

    tff2: t_flip_flop
        port map (clock => clock,
            clear => clear,
            enable => and_signals(2), -- O terceiro flip-flop alterna quando os dois anteriores
estiverem em '1'

```

```
Q => Q_internal(2)
);
```

```
-- AND para o próximo flip-flop
and_signals(3) <= and_signals(2) AND Q_internal(2);
```

```
tff3: t_flip_flop
  port map (clock => clock,
            clear => clear,
            enable => and_signals(3),
            Q => Q_internal(3)
            );
```

```
and_signals(4) <= and_signals(3) AND Q_internal(3);
```

```
tff4: t_flip_flop
  port map (clock => clock,
            clear => clear,
            enable => and_signals(4),
            Q => Q_internal(4)
            );
```

```
and_signals(5) <= and_signals(4) AND Q_internal(4);
```

```
tff5: t_flip_flop
  port map (clock => clock,
            clear => clear,
            enable => and_signals(5),
            Q => Q_internal(5)
            );
```

```
and_signals(6) <= and_signals(5) AND Q_internal(5);
```

```
tff6: t_flip_flop
  port map (clock => clock,
            clear => clear,
            enable => and_signals(6),
            Q => Q_internal(6)
            );
```


```
and_signals(7) <= and_signals(6) AND Q_internal(6);
```


```
tff7: t_flip_flop
  port map (clock => clock,
            clear => clear,
            enable => and_signals(7),
            Q => Q_internal(7)
            );
```

```
-- Atribuindo a saída dos flip-flops à saída do contador
Q0 <= Q_internal(0);
  Q1 <= Q_internal(1);
  Q2 <= Q_internal(2);
  Q3 <= Q_internal(3);
  Q4 <= Q_internal(4);
  Q5 <= Q_internal(5);
  Q6 <= Q_internal(6);
  Q7 <= Q_internal(7);

end Behavioral;
```

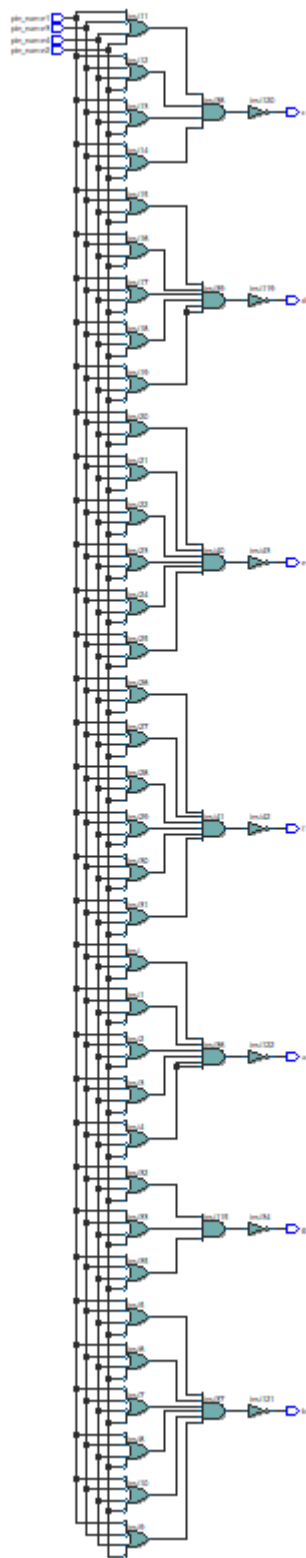2 - Representação das portas lógicas geradas pelo Quartus RTL Viewer a partir do código VHDL - Parte 1




 


## Parte 2: 16-bits counter

O contador de 16 bits descrito no código VHDL é uma unidade lógica sequencial que incrementa seu estado a cada ciclo de clock, desde que habilitado. Ele utiliza entradas como clock, clear e enable1 para controlar suas operações básicas, como contagem, reset e habilitação.
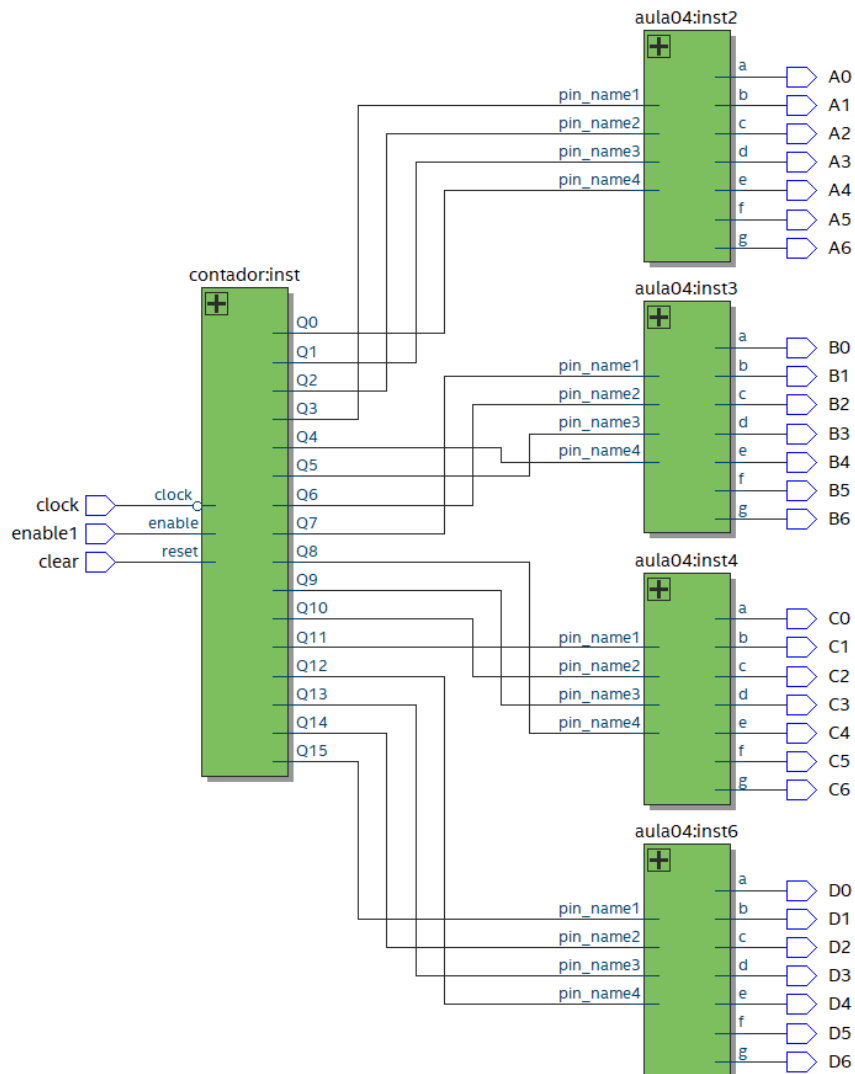
## 5 - Representação das portas lógicas geradas pelo Quartus RTL Viewer a partir do código VHDL - Parte 2



BDF da parte 2 -

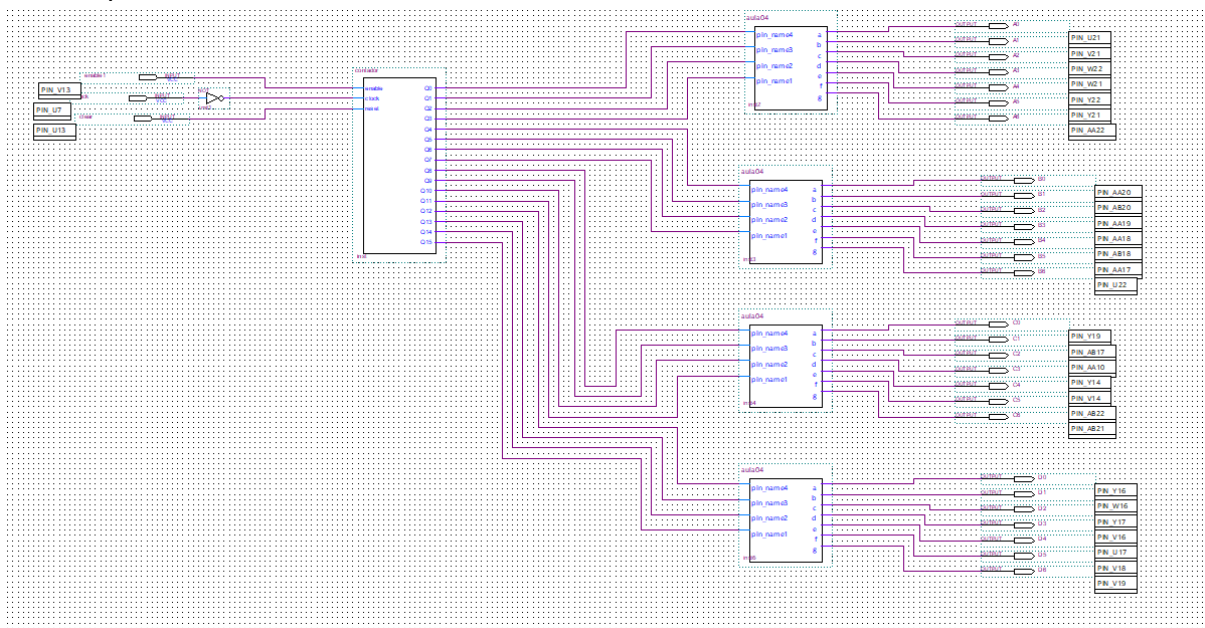

## 7- Simulação ModelSim - Parte 2

### Parte 3:

O circuito funciona como um divisor de frequência que conta até 50 milhões (50 MHz) para gerar um pulso de 1 segundo. Ao atingir 50 milhões, ele reseta e emite o sinal, que habilita um contador secundário de dígitos. Esse contador incrementa de 0 a 9, avançando a cada pulso de 1 segundo recebido do contador principal, e reseta para 0 ao atingir 9.

Um decodificador de 7 segmentos é usado para converter o valor do contador de dígitos no formato adequado para acionar um display de 7 segmentos, exibindo os números de 0 a 9.

Segue o código VHDL da parte 3:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY work;

ENTITY parte3 IS
    PORT
    (
        clock : IN STD_LOGIC;
        clear : IN STD_LOGIC;
        enable1 : IN STD_LOGIC;
        A0 : OUT STD_LOGIC;
        A1 : OUT STD_LOGIC;
        A2 : OUT STD_LOGIC;
        A3 : OUT STD_LOGIC;
        A4 : OUT STD_LOGIC;
        A5 : OUT STD_LOGIC;
        A6 : OUT STD_LOGIC
    );
END parte3;

ARCHITECTURE bdf_type OF parte3 IS

    COMPONENT contador
        PORT(enable : IN STD_LOGIC;
            clock : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            Q0 : OUT STD_LOGIC;
            Q1 : OUT STD_LOGIC;
            Q2 : OUT STD_LOGIC;
            Q3 : OUT STD_LOGIC
        );
```



END COMPONENT;

COMPONENT aula04

```
    PORT(pin_name1 : IN STD_LOGIC;
          pin_name4 : IN STD_LOGIC;
          pin_name2 : IN STD_LOGIC;
          pin_name3 : IN STD_LOGIC;
          a : OUT STD_LOGIC;
          b : OUT STD_LOGIC;
          c : OUT STD_LOGIC;
          d : OUT STD_LOGIC;
          e : OUT STD_LOGIC;
          f : OUT STD_LOGIC;
          g : OUT STD_LOGIC
    );
```

END COMPONENT;

```
SIGNAL    SYNTHESIZED_WIRE_0 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_1 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_2 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_3 : STD_LOGIC;
```

BEGIN

b2v\_inst : contador

```
PORT MAP(enable => enable1,
          clock => clock,
          reset => clear,
          Q0 => SYNTHESIZED_WIRE_1,
          Q1 => SYNTHESIZED_WIRE_3,
          Q2 => SYNTHESIZED_WIRE_2,
          Q3 => SYNTHESIZED_WIRE_0);
```

b2v\_inst2 : aula04

```
PORT MAP(pin_name1 => SYNTHESIZED_WIRE_0,
          pin_name4 => SYNTHESIZED_WIRE_1,
          pin_name2 => SYNTHESIZED_WIRE_2,
          pin_name3 => SYNTHESIZED_WIRE_3,
          a => A0,
          b => A1,
          c => A2,
          d => A3,
          e => A4,
          f => A5,
```

```
g => A6);
```

```
END bdf_type;
```

#### Parte 4:

O circuito implementado utiliza um divisor de clock para criar um atraso aproximado de 1 segundo. Isso é alcançado com a contagem de ciclos de clock até atingir um valor limite (50 milhões, considerando um clock de 50 MHz), momento em que o contador é resetado.

Um contador adicional é utilizado para rastrear a posição de exibição no display, alternando entre diferentes estados. Este contador incrementa seu valor a cada segundo e reseta após atingir 3, resultando em um ciclo de 4 estados.

A palavra "dE10" é representada em um vetor de 28 bits, onde cada caractere é codificado em 7 bits, correspondendo aos segmentos de um display de 7 segmentos. De acordo com o valor do contador, os segmentos apropriados são atribuídos aos displays HEX0 a HEX3. Assim, é criado um efeito de rotação da palavra de "direita para esquerda", exibindo os caracteres em sequência nos displays conectados.

Segue o código VHDL da parte 4:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY work;

ENTITY parte4 IS
    PORT
    (
        clock : IN  STD_LOGIC;
        clear : IN  STD_LOGIC;
        enable1 : IN  STD_LOGIC;
        A0 : OUT  STD_LOGIC;
        A1 : OUT  STD_LOGIC;
        A2 : OUT  STD_LOGIC;
        A3 : OUT  STD_LOGIC;
        A4 : OUT  STD_LOGIC;
        A5 : OUT  STD_LOGIC;
        A6 : OUT  STD_LOGIC;
        B0 : OUT  STD_LOGIC;
        B1 : OUT  STD_LOGIC;
        B2 : OUT  STD_LOGIC;
        B3 : OUT  STD_LOGIC;
```

```

B4 : OUT STD_LOGIC;
B5 : OUT STD_LOGIC;
B6 : OUT STD_LOGIC;
C0 : OUT STD_LOGIC;
C1 : OUT STD_LOGIC;
C2 : OUT STD_LOGIC;
C3 : OUT STD_LOGIC;
C4 : OUT STD_LOGIC;
C5 : OUT STD_LOGIC;
C6 : OUT STD_LOGIC;
D0 : OUT STD_LOGIC;
D1 : OUT STD_LOGIC;
D2 : OUT STD_LOGIC;
D3 : OUT STD_LOGIC;
D4 : OUT STD_LOGIC;
D5 : OUT STD_LOGIC;
D6 : OUT STD_LOGIC

```

```

);
END parte4;

```

ARCHITECTURE bdf\_type OF parte4 IS

COMPONENT palavra04

```

    PORT(enable : IN STD_LOGIC;
          clock : IN STD_LOGIC;
          reset : IN STD_LOGIC;
          Q0 : OUT STD_LOGIC;
          Q1 : OUT STD_LOGIC;
          Q2 : OUT STD_LOGIC;
          Q3 : OUT STD_LOGIC;
          Q4 : OUT STD_LOGIC;
          Q5 : OUT STD_LOGIC;
          Q6 : OUT STD_LOGIC;
          Q7 : OUT STD_LOGIC;
          Q8 : OUT STD_LOGIC;
          Q9 : OUT STD_LOGIC;
          Q10 : OUT STD_LOGIC;
          Q11 : OUT STD_LOGIC;
          Q12 : OUT STD_LOGIC;
          Q13 : OUT STD_LOGIC;
          Q14 : OUT STD_LOGIC;
          Q15 : OUT STD_LOGIC

```

```

    );
END COMPONENT;

```

COMPONENT aula04

```

    PORT(pin_name1 : IN STD_LOGIC;
          pin_name4 : IN STD_LOGIC;

```

```

        pin_name2 : IN STD_LOGIC;
        pin_name3 : IN STD_LOGIC;
        a : OUT STD_LOGIC;
        b : OUT STD_LOGIC;
        c : OUT STD_LOGIC;
        d : OUT STD_LOGIC;
        e : OUT STD_LOGIC;
        f : OUT STD_LOGIC;
        g : OUT STD_LOGIC
    );
END COMPONENT;

SIGNAL    SYNTHESIZED_WIRE_0 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_1 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_2 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_3 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_4 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_5 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_6 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_7 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_8 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_9 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_10 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_11 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_12 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_13 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_14 : STD_LOGIC;
SIGNAL    SYNTHESIZED_WIRE_15 : STD_LOGIC;

BEGIN

b2v_inst : palavra04
PORT MAP(enable => enable1,
        clock => clock,
        reset => clear,
        Q0 => SYNTHESIZED_WIRE_1,
        Q1 => SYNTHESIZED_WIRE_3,
        Q2 => SYNTHESIZED_WIRE_2,
        Q3 => SYNTHESIZED_WIRE_0,
        Q4 => SYNTHESIZED_WIRE_5,
        Q5 => SYNTHESIZED_WIRE_7,
        Q6 => SYNTHESIZED_WIRE_6,
        Q7 => SYNTHESIZED_WIRE_4,
        Q8 => SYNTHESIZED_WIRE_9,
        Q9 => SYNTHESIZED_WIRE_11,

```

```
Q10 => SYNTHESIZED_WIRE_10,  
Q11 => SYNTHESIZED_WIRE_8,  
Q12 => SYNTHESIZED_WIRE_13,  
Q13 => SYNTHESIZED_WIRE_15,  
Q14 => SYNTHESIZED_WIRE_14,  
Q15 => SYNTHESIZED_WIRE_12);
```

b2v\_inst2 : aula04

```
PORT MAP(pin_name1 => SYNTHESIZED_WIRE_0,  
         pin_name4 => SYNTHESIZED_WIRE_1,  
         pin_name2 => SYNTHESIZED_WIRE_2,  
         pin_name3 => SYNTHESIZED_WIRE_3,  
         a => A0,  
         b => A1,  
         c => A2,  
         d => A3,  
         e => A4,  
         f => A5,  
         g => A6);
```

b2v\_inst3 : aula04

```
PORT MAP(pin_name1 => SYNTHESIZED_WIRE_4,  
         pin_name4 => SYNTHESIZED_WIRE_5,  
         pin_name2 => SYNTHESIZED_WIRE_6,  
         pin_name3 => SYNTHESIZED_WIRE_7,  
         a => B0,  
         b => B1,  
         c => B2,  
         d => B3,  
         e => B4,  
         f => B5,  
         g => B6);
```

b2v\_inst4 : aula04

```
PORT MAP(pin_name1 => SYNTHESIZED_WIRE_8,  
         pin_name4 => SYNTHESIZED_WIRE_9,  
         pin_name2 => SYNTHESIZED_WIRE_10,  
         pin_name3 => SYNTHESIZED_WIRE_11,  
         a => C0,  
         b => C1,  
         c => C2,  
         d => C3,  
         e => C4,  
         f => C5,  
         g => C6);
```

b2v\_inst6 : aula04

```
PORT MAP(pin_name1 => SYNTHESIZED_WIRE_12,  
          pin_name4 => SYNTHESIZED_WIRE_13,  
          pin_name2 => SYNTHESIZED_WIRE_14,  
          pin_name3 => SYNTHESIZED_WIRE_15,  
          a => D0,  
          b => D1,  
          c => D2,  
          d => D3,  
          e => D4,  
          f => D5,  
          g => D6);
```

END bdf\_type;